

**Kathmandu University**  
**Department of Computer Science and Engineering**  
**Dhulikhel, Kavre**



A Report on '**Lab Work 2** [COMP 306]  
**Half Adder and Full Adder**

**Submitted by:**

Chandan Kumar Mahato (31)

III-year, II semester

**Submitted to:**

Prof. Dr. Sudan Jha

Department of Computer Science and Engineering

**Submission Date:** April 21, 2023

## ***Qlab1***

### ***1. Design Half Adder and Full Adder using proteus simulation.***


#### **Objective:**

To Design Half Adder and Full Adder


#### **Components Required:**

- Probe
- Wire
- Gates (AND, XOR, OR)
- Digital Constant

#### **Circuit Diagram**

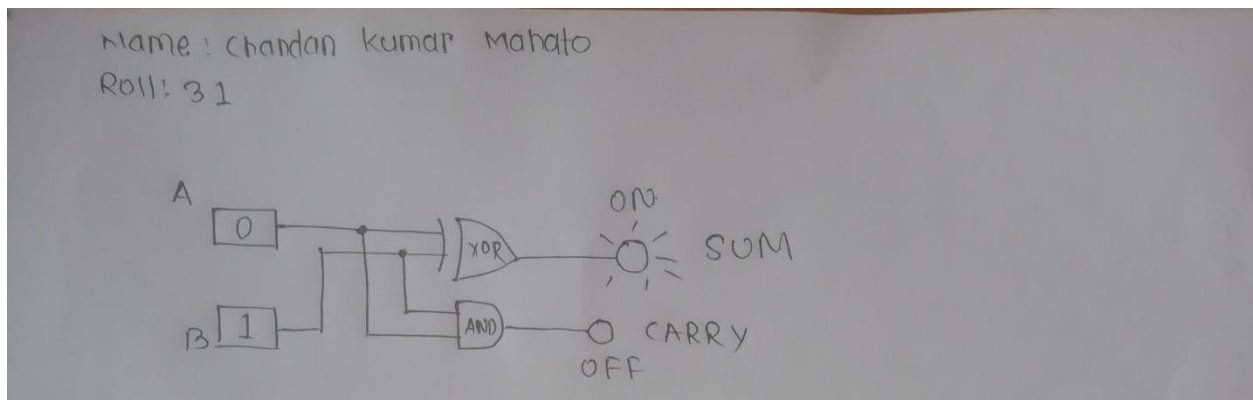

***Fig 1: Half-Adder Circuit***

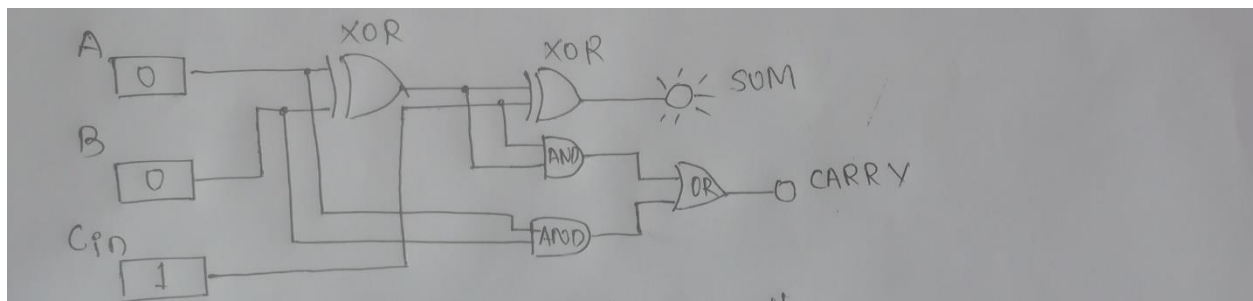

***Fig 2: Full-Adder Circuit***

### Truth Table:

The truth table obtained for the Half Adder and Full Adder after varying their input parameters during simulation are shown in the table below:

Chandan Kumar Mahato  
Roll: 31

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Fig 3: Truth Table Half-Adder



A	B	Cin	Sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Fig 4: Truth Table Full-Adder

## Conclusion:

Both Half Adder and Full Adder were successfully simulated using Proteus Simulation and the truth tables were determined by checking multiple combinations of inputs and their effects on the probe.

## Screenshots:

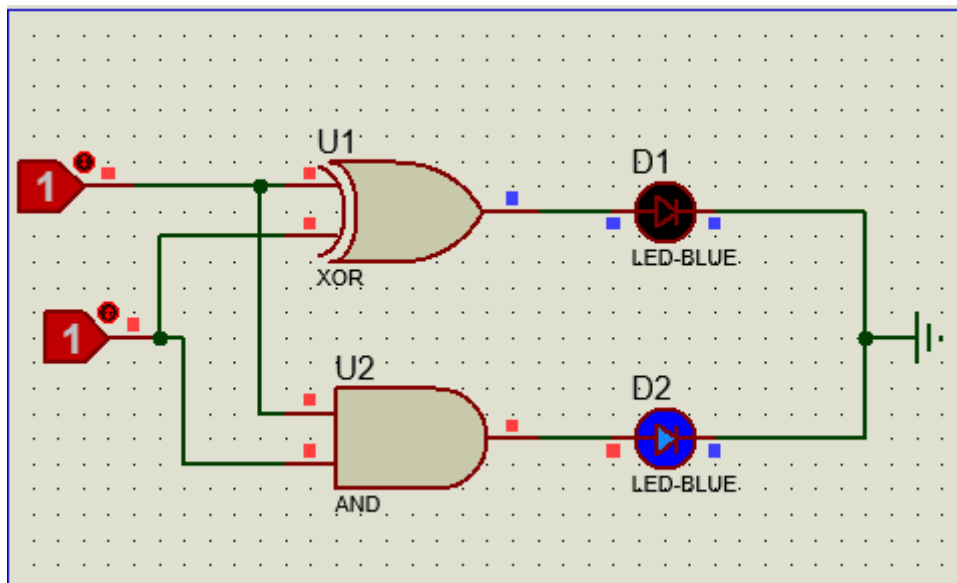 

*Fig 5: half-adder Circuit*

 
 


Fig 6: Full-adder Circuit